

ELECTROMAGNETIC

INDUCTION

classmate

Date _____

Page _____

01/02/2023

FARADAY'S LAWS

When Φ_B through a loop changes, an emf is induced in the loop which lasts as long as the Φ_B changes.
(magnetic flux)

$$E = -\frac{d\Phi_B}{dt}$$

where

$$\Phi_B = \int_S \vec{B} \cdot d\vec{s}$$

NOTE:

$$\oint_S \vec{B} \cdot d\vec{s} = 0 \Rightarrow$$



Magnetic flux through a closed surface is ZERO

\Rightarrow \nexists Magnetic monopole

REMARK: - sign in FL, indicates the emf produced opposes change of Φ_B .

- Lenz's law - Induced current in a loop will oppose the very cause responsible for inducing current.

eg -

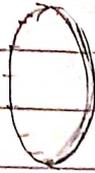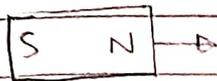

If N is moved towards the fixed loop,

$$\frac{d\phi_B}{dt} \uparrow$$

To oppose this change, current is induced s.t. $\frac{d\phi_B}{dt} \downarrow$. i.e. face of loop on

magnet's side would act like N pole.

Hence anti clockwise current is induced.

Since
$$\phi_B = \vec{B} \cdot \vec{A}$$

$$= B \cdot A \cos \theta$$


To change ϕ_B , we can change any of the 3 qty.

Motional emf - A or $\cos \theta$ changes

Time varying B - B changes.

Motional emf is induced only in conductors, whereas emf is induced in space itself in case of time varying B.

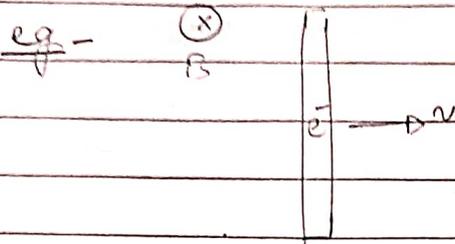Reason : Cause of motional emf is the force on free e^- , which causes change in charge distribution & development of \vec{E} , hence inducing emf.




Due to motion of rod, e^- acquires vel. v .

So, it experiences a force $e(\vec{v} \times \vec{B})$



Accumulation of charges creates E .

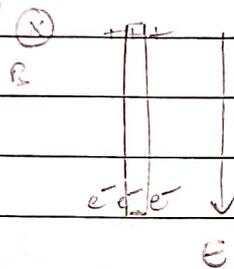

In eq.

$$-e\vec{E} + (-e)(\vec{v} \times \vec{B}) = 0$$

$$\Rightarrow \vec{E} = -(\vec{v} \times \vec{B})$$


This V acts as induced emf in conductor.

$$dV = -\vec{E} \cdot d\vec{l}$$

$$\Rightarrow V = \int (\vec{v} \times \vec{B}) \cdot d\vec{l}$$

When B, v, l are mutually \perp ,

$$E = Blv$$

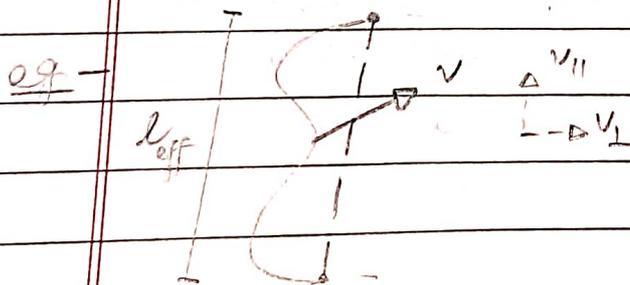


$$E = B l_{\perp} v_{\perp}$$

$B \perp$ to plane of motion


NOTE: if $\vec{B} \parallel \vec{v}$
 $\vec{B} \parallel \vec{l}$
 $\vec{v} \parallel \vec{l}$ } $\rightarrow E=0$ (property of scalar triple product)

Q

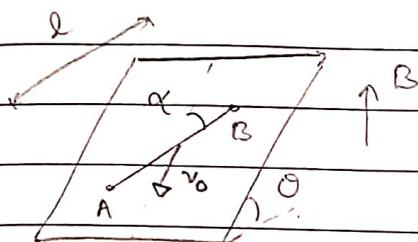


Find E & end which is a greater potential

A.

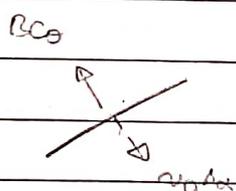


$$E = (B \cos \alpha) (v \sin \alpha) (l)$$
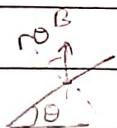
$$= \underline{B v l \sin \alpha \cos \alpha}$$



A is at greater potential.

Q

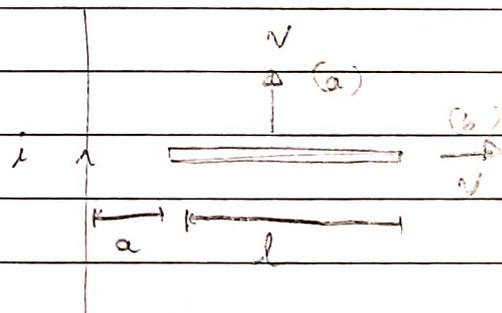


Find E in cases (a) & (b)

A b) $E=0$ since $\vec{v} \parallel \vec{l}$

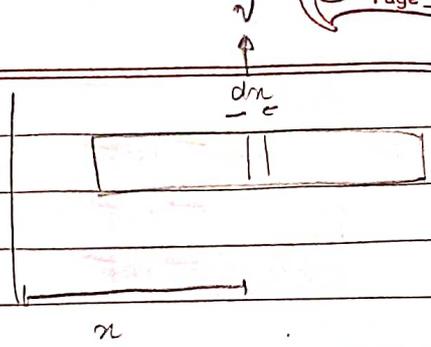a) $\vec{v} \parallel \vec{B} \parallel \vec{l}$ but B is diff. for diff. pts.

$$B_{\cancel{x}} = \left(\frac{\mu_0}{2\pi} \right) \left(\frac{i}{r} \right)$$




$$d\epsilon = B_{\cancel{x}} \nu \, d\cancel{x}$$

$$= \left(\frac{\mu_0 i \nu}{2\pi} \right) \left(\frac{d\cancel{x}}{r} \right)$$

$$\epsilon = \int_{\cancel{x}=a}^{\cancel{x}=a+l} d\epsilon = \frac{\mu_0 i \nu}{2\pi} l \left(1 + \frac{l}{a} \right)$$

Q. $\otimes B$ Find ϵ .

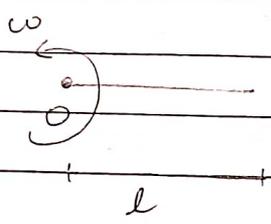


A.


$$d\epsilon = B \nu \, d\cancel{x} = B \omega r \, d\cancel{x}$$

$$\epsilon = \int_{\cancel{x}=0}^{\cancel{x}=l} d\epsilon = \frac{B \omega r^2}{2}$$

Q. Find ϵ when rod at θ

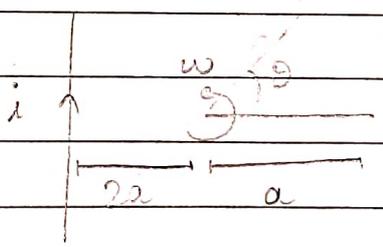

A.

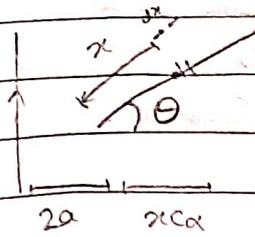

$$d\mathcal{E} = B_m v_m dx$$

$$= \left(\frac{\mu_0 i}{2\pi} \right) \left(\frac{1}{2a+x} \right) (v 2x) dx$$


$$\mathcal{E} = \int_{x=0}^{x=2a} d\mathcal{E} = \frac{\mu_0 i v}{2\pi C_0} \int_0^{2a} \frac{2x}{2a+x} dx$$

$$= \left(\frac{\mu_0 i v}{2\pi C_0} \right) \left(a - \frac{2a}{C_0} \ln \left(\frac{1+C_0}{2} \right) \right)$$

03/08/2023

A conductor moving in \vec{B} will act as battery for a circuit

Q.

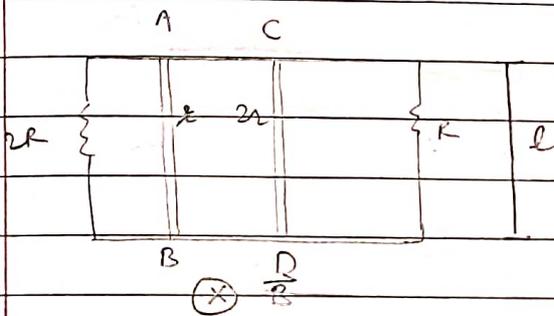

Find current through each resistor & rod A if both rods moving with same speed v

a) in same dirⁿ

b) in opp. dirⁿ


A.

a) $\mathcal{E}_{AC} = Bvl$

$\mathcal{E}_{CD} = Bvl$

$$\mathcal{E}_{eq} = \frac{Bvl}{\frac{1}{\lambda} + \frac{1}{2r} + \frac{1}{R} + \frac{1}{2r}} = \frac{3Bvl}{2r}$$

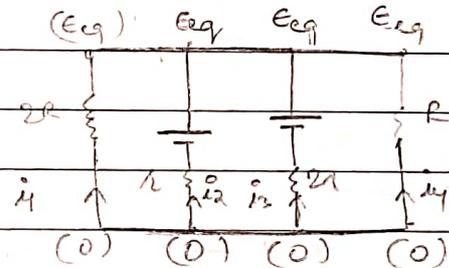
$$= \left(\frac{BvlR}{\lambda r} \right) \frac{3R+3r}{2r}$$



$i_1 = \frac{Bvl}{2(\lambda r)}$ $i_2 = \frac{\frac{BvlR}{\lambda r} - Bvl}{\lambda} = -\left(\frac{Bvl}{\lambda r} \right)$ $i_3 = \frac{-Bvl}{2(\lambda r)}$ $i_4 = \frac{Bvl}{(\lambda r)}$

$$b) E_{eq} = \frac{BvL}{1} - \frac{BvL}{2R}$$

$$= \frac{BvLR}{3(4R)}$$

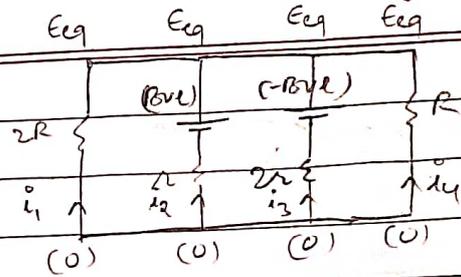


$$i_1 = \frac{BvL}{6(4R)}$$

$$i_2 = \frac{-BvL(31-2R)}{3(4R)}$$

$$i_3 = \frac{-BvL(31+4R)}{6(4R)}$$

$$i_4 = \frac{BvL}{3(4R)}$$

Q


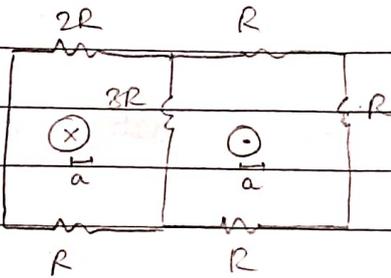


$\frac{dB}{dt} = \alpha$ in both regions.

Find current through each resistor

A
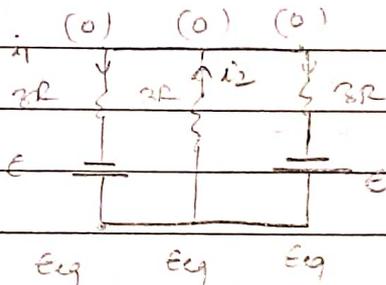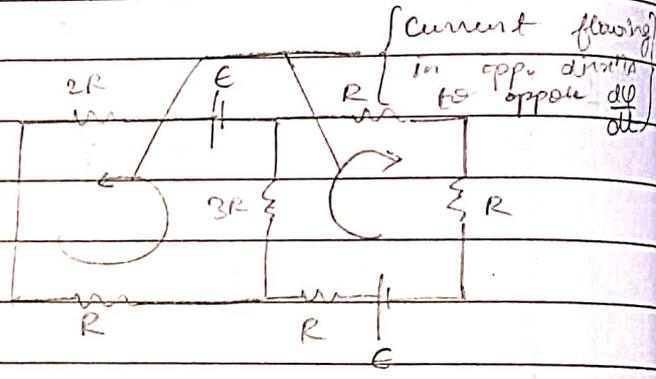
$$\frac{d\phi}{dt} = \pi a^2 \alpha \implies$$




* We can represent induced emf with a battery anywhere in circuit except the common side

$$E_{eq} = \frac{E}{\frac{1}{2R} + \frac{1}{2R} + \frac{1}{2R}} = \frac{2E}{3}$$


$$i_1 = i_3 = \frac{E}{9R} = \left(\frac{\pi a^2 \alpha}{9R} \right)$$
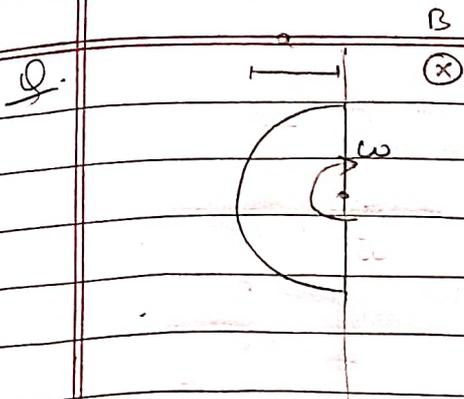
$$i_2 = \frac{2E}{9R} = \frac{2\pi a^2 \alpha}{9R}$$





Find induced in the loop as a fun of time.

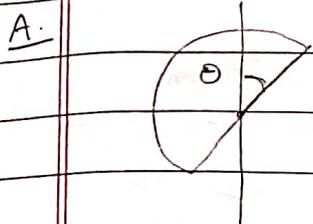Also draw the graph b/w induced emf & time.




$$A = \frac{a^2 \theta}{2} = \left(\frac{a^2 \omega t}{2} \right)$$
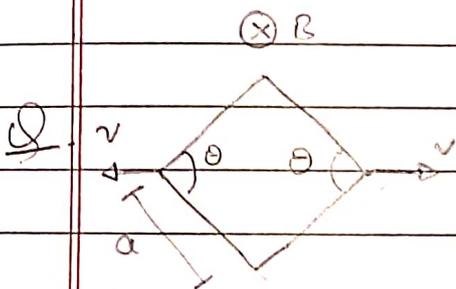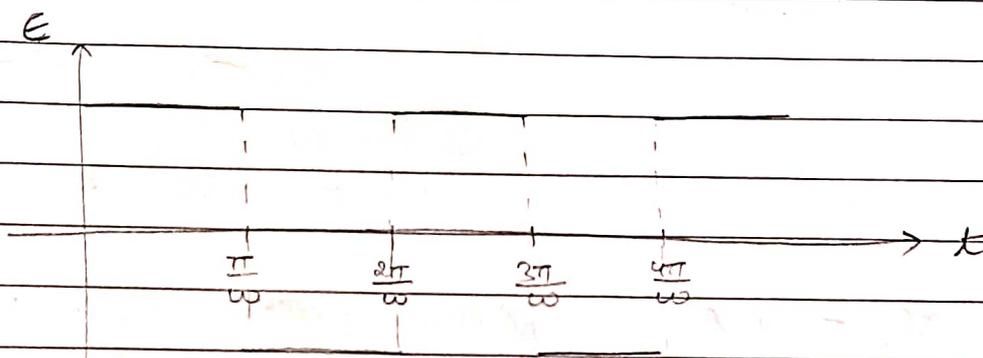
$$\frac{d\phi}{dt} = \frac{d(BA)}{dt} = \frac{Ba^2}{2} \left(\frac{d\theta}{dt} \right) = \left(\frac{Ba^2 \omega}{2} \right)$$



Find induced when θ reduces to 60° .

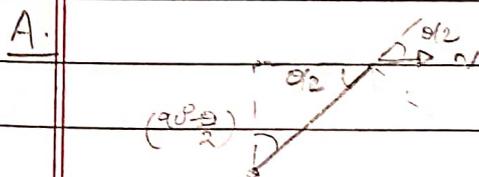

$$A = 2 \left(a \cos \frac{\theta}{2} \right) \left(a \sin \frac{\theta}{2} \right) = a^2 \cos \theta$$


$$v = \frac{d(a^2 \cos \theta)}{dt} = -\frac{a^2 \sin \theta}{2} \left(\frac{d\theta}{dt} \right)$$

$$\begin{aligned} \frac{d\phi}{dt} &= \frac{d(B \cdot a^2 \cos \theta)}{dt} = a^2 B \cos \theta \frac{d\theta}{dt} \\ &= -2avB \cos \theta \left(\frac{d\theta}{dt} \right) \end{aligned}$$

- Total charge flowing through loop -

$$i = \frac{\epsilon}{R} \Rightarrow \frac{dq}{dt} = \frac{d\phi}{R dt} \Rightarrow q = \int \frac{d\phi}{R}$$

$$= \frac{\Delta\phi}{R}$$

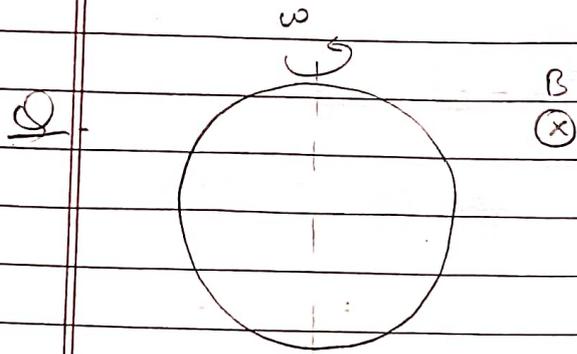

Find net charge that flows through the ring if it rotates through an angle

- a) $\pi/2$ b) π c) 2π

about one of its diameters.


A. $\phi_i = BA$ (area vector assumed in direction of B)

a) $\phi_f = 0 \Rightarrow q = -\left(\frac{BA}{R}\right)$

b) $\phi_f = -BA \Rightarrow q = -\left(\frac{2BA}{R}\right)$

c) $\phi_f = BA \Rightarrow q = 0$

Q.

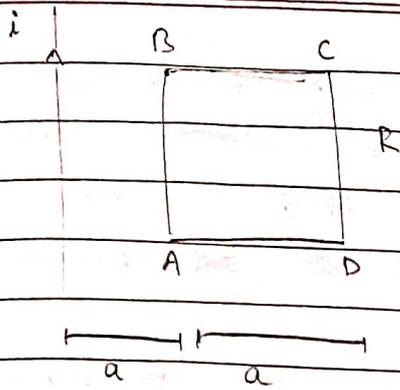

Find charge that flows through the sq. loop if it is turned about AB through


a) 90°

b) 120°

A.

$$\phi_i = \int d\phi = \int_a^{2a} \left(\frac{\mu_0}{2\pi} \right) \left(\frac{i}{r} \right) a dr$$

$$= \frac{\mu_0 i a l(2)}{2\pi}$$

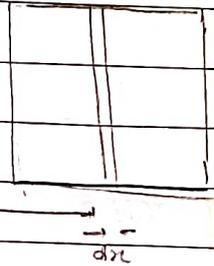


a) $\phi_f = \int d\phi = \int B(a dr) \cos \theta$

$$= \int_0^a \left(\frac{\mu_0}{2\pi} \right) \left(\frac{i a}{\sqrt{r^2 + a^2}} \right) \frac{r}{\sqrt{r^2 + a^2}} dr$$

$$= \frac{\mu_0 i a}{4\pi} \left[l(\sqrt{r^2 + a^2}) \right]_0^a$$


$$= \frac{\mu_0 i a l(2)}{4\pi}$$

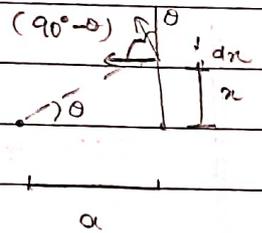

$r = a \tan \theta$
 $\Rightarrow dr = a \sec^2 \theta d\theta$

$\Rightarrow q = \frac{\phi_f - \phi_i}{R} = -\frac{\mu_0 i a l(2)}{4\pi R}$


b)

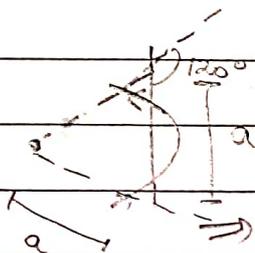

By sym., $\phi_f = 0$

$\Rightarrow q = \frac{\phi_f - \phi_i}{R} = -\frac{\mu_0 i a l(2)}{2\pi R}$

04/08/2022

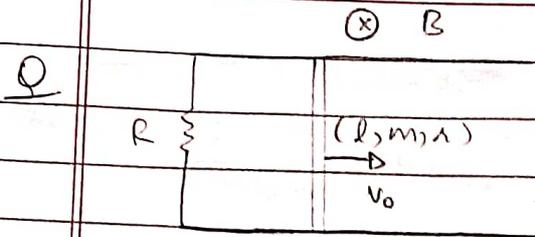


The rod is pulled ||
to rails with const. vel. v_0
then find

- current in circuit
- V across rod
- force req. to move the rod with consto vel.

A (i) $\epsilon = Bv_0l \Rightarrow i = \frac{Bv_0l}{R+r}$

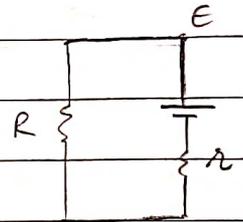(ii) $V = \epsilon - ir = \frac{(Bv_0l)(R)}{(R+r)}$



(iii) $F_B = F_{ext}$

$$F_B = ilB = \frac{B^2v_0l^2}{(R+r)}$$

$$\begin{aligned} \therefore F_{ext} &= F_B \\ &= \frac{B^2v_0l^2}{(R+r)} \end{aligned}$$

Q In the above Q, if rod is projected with vel. v_0 || to the rails, then find vel. of rod.

- as a fnⁿ of time
- as a fnⁿ of dist covered

A $F_B = \frac{B^2l^2}{(R+r)} v \Rightarrow a = -\frac{B^2l^2}{(R+r)m} v$

$$\Rightarrow \int_{v_0}^v \frac{dv}{v} = \int_0^t -\frac{B^2l^2}{(R+r)m} dt$$

$$\Rightarrow v = v_0 e^{-\frac{B^2 l^2}{m(R+r)} t}$$

$$\int_0^x dx = \int_0^t v_0 e^{-\frac{B^2 l^2}{m(R+r)} t} dt$$


$$\Rightarrow x = \frac{v_0 m(R+r)}{B^2 l^2} \left[1 - e^{-\frac{B^2 l^2}{m(R+r)} t} \right]$$

$$\Rightarrow x = \frac{m(R+r)}{B^2 l^2} (v_0 - v)$$

$$\Rightarrow v = v_0 - \frac{B^2 l^2}{m(R+r)} x$$

Q. In the above Q, if a force of const. mag. is applied on rod at rest. Find v as a funⁿ of time & v_{max} .

A.

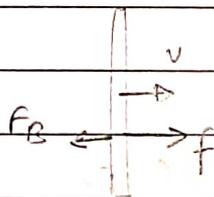

(force of const mag.)


$$a = -\frac{(F_B - f)}{m} = -\frac{B^2 l^2}{m(R+r)} v + \left(\frac{f}{m}\right)$$

$$\Rightarrow \frac{dv}{dt} + \frac{B^2 l^2}{m(R+r)} v = \left(\frac{f}{m}\right)$$

$$\Rightarrow v = \frac{f(R+r)}{B^2 l^2} \left[1 - e^{-\frac{B^2 l^2}{m(R+r)} t} \right]$$

$$v_{max} = \frac{f(R+r)}{B^2 l^2}$$


at v_{max} $F_B = f$

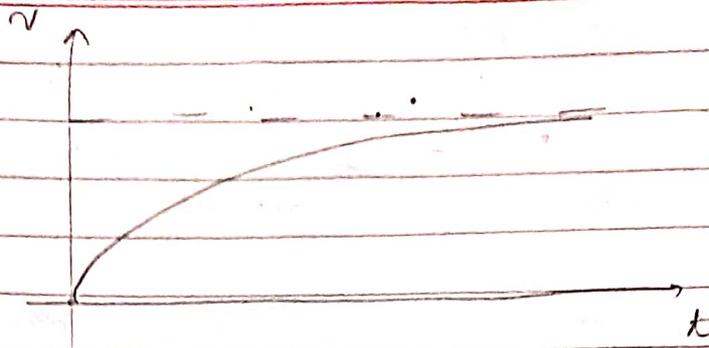

$$v = v_{\max} (1 - e^{-\lambda t})$$

$$\lambda = \frac{B^2 l^2}{f(R + \lambda)}$$


Q.

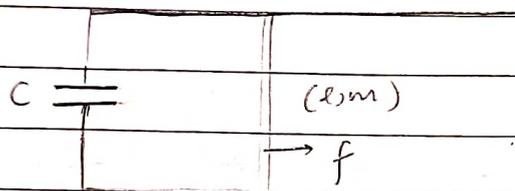

Resistance less circuit.
Conducting rod
initially at rest.

Find v of rod & charge on cap.
as a fun of time.

A.

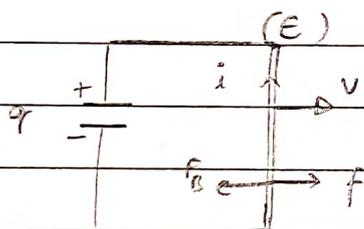


$$q = EC = (Blc) v$$

$$i = \frac{dq}{dt} = (Blc) \left(\frac{dv}{dt} \right) = (Blc) (a)$$


$$a = - \frac{(F_B - f)}{m} = - \frac{ilB}{m} + \frac{f}{m} = - \frac{B^2 l^2 c a}{m} + \frac{f}{m}$$

$$\Rightarrow a = \left(\frac{f}{m + B^2 l^2 c} \right) \Rightarrow v = \left(\frac{f t}{m + B^2 l^2 c} \right)$$

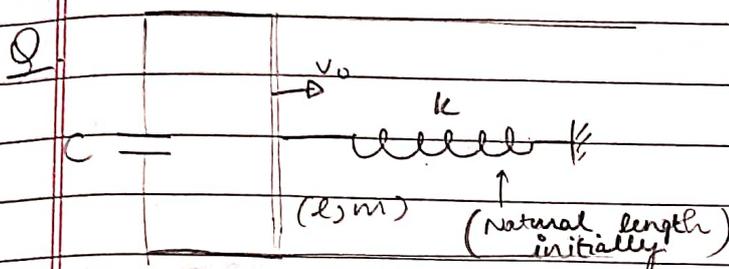NOTE: If instead, rod was projected with v_0 & no ext force was applied, the cap. would charge instant \Rightarrow no current flown in circuit \Rightarrow rod moves unaffected.



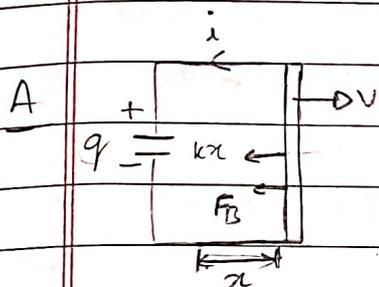P.T rod will exhibit SHM.
Find T & A of SHM.



$$q = EC = (Blc)v$$

$$\Rightarrow i = \frac{dq}{dt} = (Blc) \left(\frac{dv}{dt} \right) = (Blc)(-a)$$

$$a = - \frac{(F_B + kx)}{m} = - \frac{i l B}{m} - \frac{k x}{m}$$

$$\Rightarrow a \left(1 + \frac{B^2 l^2 c}{m} \right) = - \frac{k x}{m}$$

$$\Rightarrow \ddot{x} = - \left(\frac{k}{m + B^2 l^2 c} \right) x$$

□

$$T = 2\pi \sqrt{\frac{m + B^2 l^2 c}{k}}$$

$$v_0 = A\omega = A \sqrt{\frac{k}{m + B^2 l^2 c}}$$


$$\Rightarrow A = v_0 \sqrt{\frac{m + B^2 l^2 c}{k}}$$

Energy Method

$$\frac{1}{2}mv^2 + \frac{1}{2}kx^2 + \frac{1}{2}Cv^2 = \text{const.}$$

↓
(Bvl)²

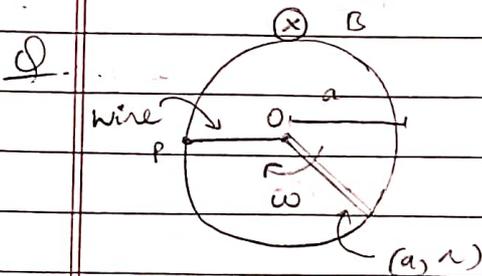
$$\Rightarrow \left(\frac{m + B^2 l^2 C}{2} \right) v^2 + \frac{k}{2} x^2 = \text{const.} \Rightarrow T = 2\pi \sqrt{\frac{m + B^2 l^2 C}{k}}$$




Resistance of ring is R .
Find current in rod as a fnⁿ of angle b/w rod & OP.

Also find the torque of Lenz force about the pivot.

A.

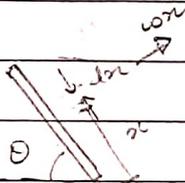
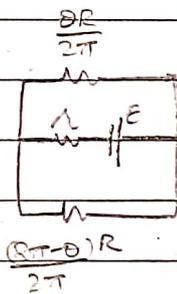
$$E = \int Bv dx = \int_0^a Bv \sin \theta dx = \frac{Bva^2}{2}$$



$$E_{eq} = \frac{E}{R} = \frac{ER}{R + \frac{4\pi^2 l}{\theta(2\pi - \theta)}}$$

$$i = \frac{E - E_{eq}}{R} = \frac{4\pi^2}{\theta(2\pi - \theta)} \left(\frac{E}{R + \frac{4\pi^2 l}{\theta(2\pi - \theta)}} \right)$$

$$= \frac{Bva^2}{\left(\frac{\theta(2\pi - \theta)R + 4\pi^2 l}{\theta(2\pi - \theta)} \right)}$$

$$i_{\text{max}} = \frac{Bva^2}{2l} \quad (\theta = 0)$$

$$i_{\text{min}} = \frac{2Bva^2}{R + 4l} \quad (\theta = \pi)$$


* only when line of action of force \perp rod

classmate

Date _____
Page _____

$$\int_0^a d\tau = \int_0^a (iBdx)(x) \Rightarrow \tau = \frac{Bia^2}{2} = (Bi a) \left(\frac{a}{2}\right)^*$$


\uparrow F_B \uparrow (dist of centre)

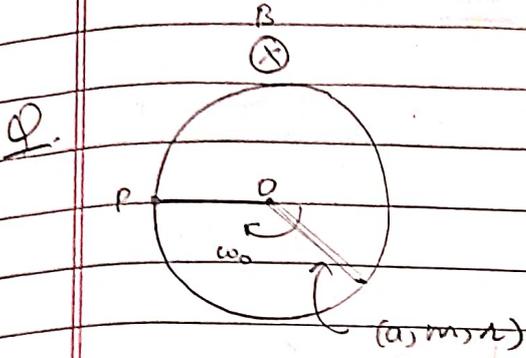

Resistance less rim.

Rod is projected with ω_0 .
Find ω of rod as a funⁿ of time & angle rotated

A

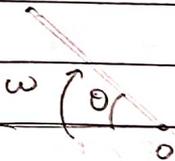

$$E = \int B\omega x dx = \frac{B\omega a^2}{2}$$

$$i = \frac{E}{R} = \frac{B\omega a^2}{2R}$$

$$\tau = \left(\frac{-Ba^2}{2}\right) i = \left(\frac{-B^2 a^4}{4R}\right) \omega \Rightarrow \left(\frac{ml^2}{3}\right) (\alpha) = \left(\frac{-B^2 a^4}{4R}\right) \omega$$

$$\Rightarrow \int_{\omega_0}^{\omega} \frac{d\omega}{\omega} = \int_0^t \frac{-3B^2 a^4}{4ml^2 R} dt$$


$$\Rightarrow \omega = \omega_0 e^{\frac{-3B^2 a^4 t}{4ml^2 R}}$$

$$\Rightarrow \int_0^{\theta} d\theta = \int_0^t \omega_0 e^{-\lambda t} dt \Rightarrow \theta = \frac{\omega_0}{\lambda} e^{-\lambda t}$$

$$\Rightarrow \omega = \lambda \theta \quad \lambda = \frac{-3B^2 a^4}{4ml^2 R}$$

Q. In the above Q, if const. F applied at centre, find ω as a fⁿ of t.

A.

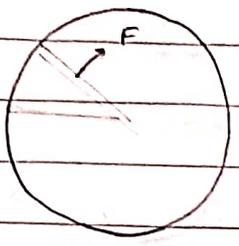


$$\tau = \frac{Fa}{2} - \left(\frac{\beta^2 a^4}{4I} \right) \omega$$

$$\Rightarrow \left(\frac{ml^2}{3} \right) \left(\frac{d\omega}{dt} \right) + \left(\frac{\beta^2 a^4}{4I} \right) \omega = \left(\frac{Fa}{2} \right)$$

$$\tau_0 = \left(\frac{Fa}{2} \right)$$


$$\omega = \frac{2\tau F}{\beta^2 a^3} \left(1 - e^{-\frac{3\beta^2 a^4 t}{4Iml^2}} \right)$$

Q.

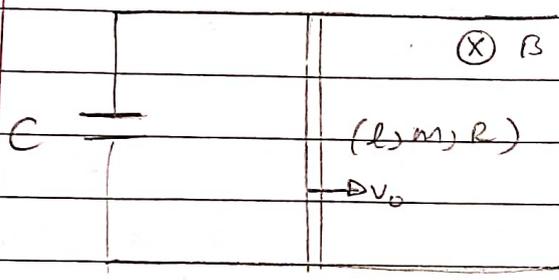

Find charge on cap., current in circuit & force req. to move rod with const. vel. as a fⁿ of time.

A.

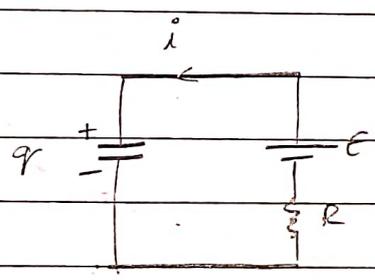

$$-\frac{q}{C} - iR + E = 0$$

$$\Rightarrow R \frac{dq}{dt} + \frac{q}{C} = E$$


$$\Rightarrow \underline{q = EC \left(1 - e^{-\frac{t}{RC}} \right)}$$

$$i = \frac{E}{R} e^{-\frac{t}{RC}}, \quad E = Bvl$$

$$F = iBl = \frac{EBl}{R} e^{-\frac{t}{RC}}$$

Q. In the above Q, if rod projected with v_0 , find charge on cap. & current in circuit as a fun of time.

A.

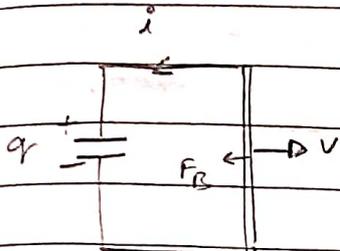

$$-\frac{q}{C} - iR + \epsilon = 0$$

$$\Rightarrow R \frac{dq}{dt} + \frac{q}{C} = Blv$$

$$\Rightarrow R \frac{d^2q}{dt^2} + \frac{dq}{dt} = Bl \frac{dv}{dt}$$

$$a = \frac{-F_B}{m} = \frac{-ilB}{m}$$

$$\Rightarrow R \frac{d^2q}{dt^2} + \frac{dq}{dt} = Bl \left(-\frac{Bl}{m} \right) \left(\frac{dq}{dt} \right)$$

$$\Rightarrow \frac{dv}{dt} = -\left(\frac{Bl}{m} \right) \left(\frac{dq}{dt} \right)$$

$$\Rightarrow \frac{d^2q}{dt^2} = -\left(\frac{1 + B^2 l^2}{RC} \right) \left(\frac{1}{R} \right) \left(\frac{dq}{dt} \right)$$

$$\Rightarrow \frac{di}{dt} = -\left(\frac{1 + B^2 l^2}{RC} \right) i$$

$$\Rightarrow \int_{i_0}^i \frac{di}{i} = \int_0^t -\left(\frac{1 + B^2 l^2}{RC} \right) dt$$

$$\Rightarrow i = i_0 e^{-\frac{1}{R} \left(\frac{1 + B^2 l^2}{C} \right) t}$$

$$i_0 = \left(\frac{Bv_0 l}{R} \right) \Rightarrow i = \left(\frac{Bv_0 l}{R} \right) e^{-\frac{1}{R} \left(\frac{1 + B^2 l^2}{C} \right) t}$$

$$\Rightarrow q = \frac{Bv_0 l}{\left(\frac{1 + B^2 l^2}{C} \right)} \left[1 - e^{-\frac{1}{R} \left(\frac{1 + B^2 l^2}{C} \right) t} \right]$$

$$\int_{v_0}^v dv = \int_0^q -\frac{Bl}{m} dq$$

$$v = v_0 - \frac{Blq}{m}$$


$$v_{\text{terminal}} = v_0 - \frac{Blq_{\text{max}}}{m} = v_0 \left[1 - \frac{B^2 l^2}{\left(\frac{m}{C} + B^2 \right)} \right]$$

$$= \left(\frac{mv_0}{m + B^2 l^2 C} \right)$$

To directly calc. v_T , we could have found v at which $i=0$.

$$\Rightarrow \frac{q}{c} = Bv \quad \& \quad v = v_0 - \frac{Bq}{m}$$

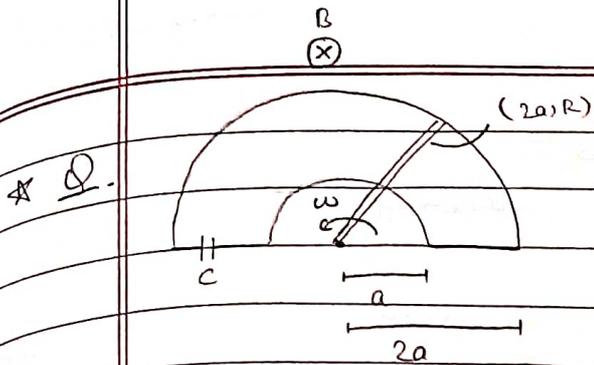
$$\Rightarrow v = v_0 - \frac{B^2 l^2 C}{m} v \Rightarrow v = \frac{mv_0}{m + B^2 l^2 C}$$



Find charge on cap.
when rod turns through θ .

A.
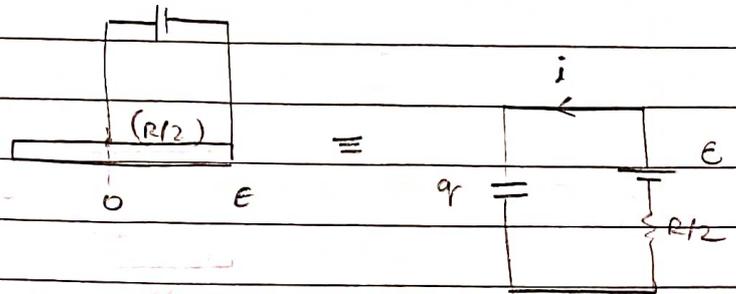
$$\mathcal{E} = \left(\frac{B\omega a^2}{2} \right)$$



$$-\frac{q}{C} - \frac{Ri}{2} + E = 0 \quad \Rightarrow \quad R \frac{dq}{dt} + \frac{2q}{C} = 2E$$

$$\Rightarrow q = EC \left(1 - e^{-\frac{2t}{RC}} \right)$$

$$\text{at } t = 0 \quad \Rightarrow \quad q = EC \left(1 - e^{-\frac{2 \cdot 0}{RC}} \right)$$


08/08/2017

INDUCED \vec{E} Produced due to time varying \vec{B} in space \vec{E} E_{induced}

- | | |
|---|--------------------------|
| - Due to charge | - Due to changing B |
| - (+ve) \rightarrow (-ve) | - Closed field lines |
| - Conservative Field
(Potential field) | - Non-conservative field |

$$\Rightarrow \oint \vec{E} \cdot d\vec{l} = 0$$
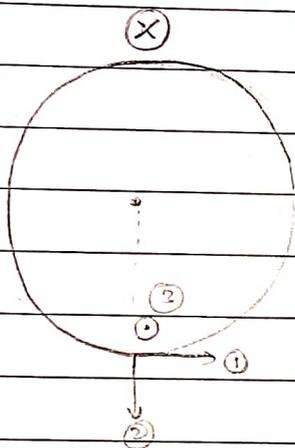
$$\oint \vec{E} \cdot d\vec{l} = - \left(\frac{d\phi}{dt} \right)$$



For determining E_i around a cylindrical \vec{B} , we use sym. argument.

We assume E_i has 3 components, ①, ②, ③ at every pt. on the circular path.

$$E_{\text{③}} = 0 \quad \text{since } E_i \perp B \quad (\text{property of } E_i)$$

$$E_{\text{②}} = 0 \quad \text{since no charge inside cylindrical surface (by Gauss law)}$$

$\Rightarrow E_i = E_{\text{①}}$ i.e. \vec{E}_i is along tangent only!


To find dirⁿ of E_i , find dirⁿ of induced current

If $r < R$

$$\oint E_i \cdot dl = \frac{d\varphi}{dt}$$

$$\Rightarrow (E_i)(2\pi r) = (\pi r^2) \left(\frac{dB}{dt} \right)$$


$$\Rightarrow E_i = \left(\frac{r}{2} \right) \left(\frac{dB}{dt} \right)$$

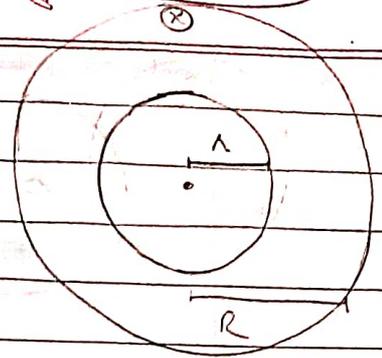If $r > R$


$$\oint E_i \cdot dl = \frac{d\varphi}{dt}$$

$$\Rightarrow (E_i)(2\pi r) = (\pi R^2) \left(\frac{dB}{dt} \right)$$

$$\Rightarrow E_i = \frac{R^2}{2r} \left(\frac{dB}{dt} \right)$$

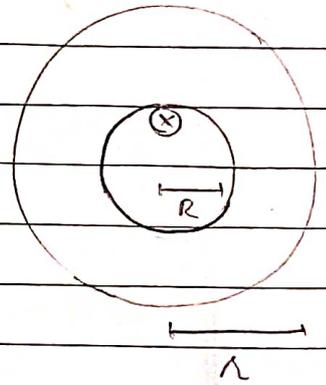If B changing with both r & t

$$\varphi = \int_0^r (2-r) (dr) (B(r, t))$$

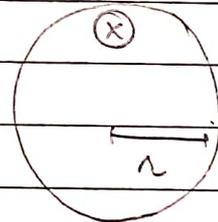
 $B(r, t)$ 

$$\oint E_i \cdot dl = \frac{\partial \varphi}{\partial t}$$

$$\Rightarrow E_i (2\pi r) = \frac{\partial \varphi}{\partial t}$$

$$\Rightarrow E_i = \left(\frac{1}{2\pi r} \right) \left(\frac{\partial \varphi}{\partial t} \right)$$


Q.

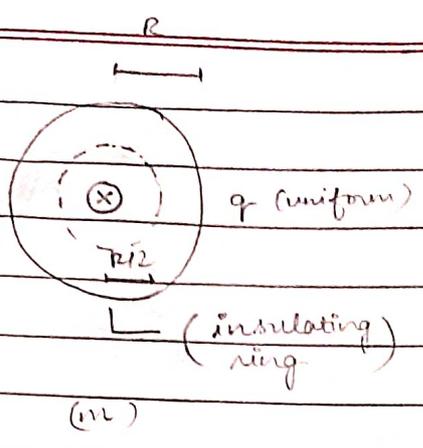

$$\frac{dB}{dt} = \alpha$$

Find angular speed of the ring after time 't' if the ring is at rest at $t=0$

A.

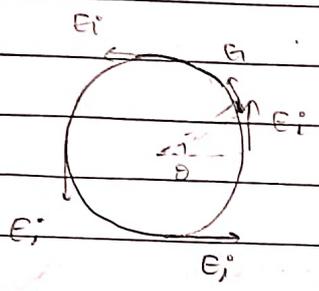

$$F_{net} = 0$$

$$d\tau = (E_i dq) (R)$$

$$\Rightarrow \tau = qE_i R$$

$$(E_i) (2\pi R) = \frac{(\pi R^2)}{4} (\alpha) \Rightarrow (mR^2) \left(\frac{d\omega}{dt} \right) = \frac{qR^2 \alpha}{8}$$

$$\Rightarrow E_i = \left(\frac{R\alpha}{8} \right) \Rightarrow \omega = \left(\frac{q\alpha}{8m} \right) t$$

Q.

In the above Q, if initially there was uniform \vec{B} & it was suddenly switched off, find angular speed acq. by ring.


A.

$$\tau = qE_i R = \left(\frac{qR^2}{8} \right) \left(\frac{dB}{dt} \right) \Rightarrow mR^2 \left(\frac{d\omega}{dt} \right) = \left(\frac{qR^2}{8} \right) \left(\frac{dB}{dt} \right)$$

$$\Rightarrow \int_0^\omega mR^2 d\omega = \int_{B_0}^0 \frac{qR^2}{8} dB$$

$$\Rightarrow \omega = - \frac{qB_0}{8m}$$


Q.

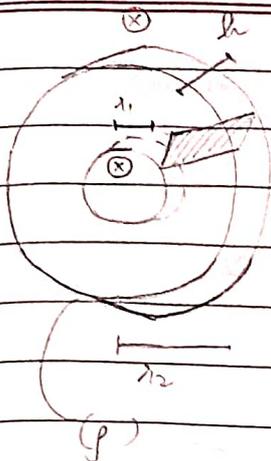

$$\frac{dB}{dt} = \alpha$$

Find current inside conductor

A.

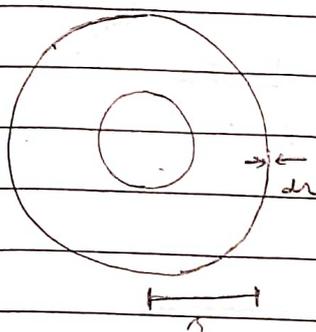

$$dR = \frac{\rho (2\pi r)}{h(dr)}$$

$$E_r = \pi r^2 \alpha$$


$$di = \frac{E_r}{dR} = \frac{\pi r^2 \alpha (h dr)}{\rho (2\pi r)}$$

$$\Rightarrow i = \frac{h\alpha}{2\rho} \int_{r_1}^{r_2} r dr = \frac{h\alpha (r_2^2 - r_1^2)}{4\rho}$$

NOTE:

If \vec{B} was given only inside, E for every elem. would have been same. In that case we could have calc. Req. (all elems. in l) & $i = E/Req$

Q

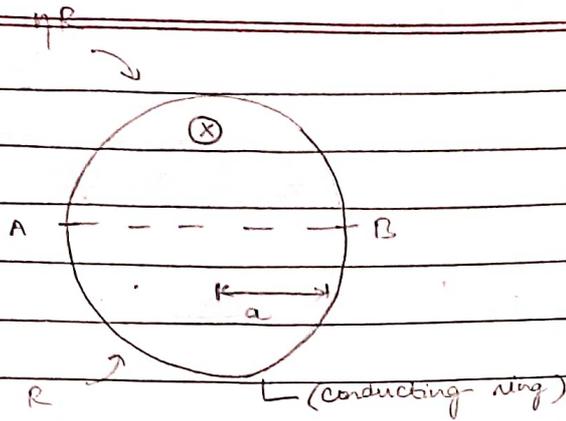


$$\frac{dB}{dt} = \alpha$$

find $V_A - V_B$

A

$$\mathcal{E} = \pi a^2 \alpha$$

→

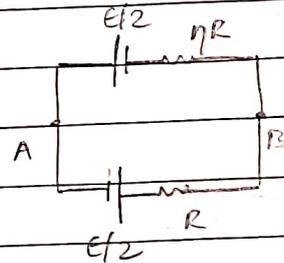


This is induced in the whole ring. It is divided uniformly along length of ring.

Since $A \rightarrow B = A \leftarrow B \Rightarrow \mathcal{E}$ is equally divided

$$\mathcal{E}_{eq} = \frac{\frac{\mathcal{E}}{2\eta R} - \frac{\mathcal{E}}{2R}}{\frac{1}{\eta R} + \frac{1}{R}} = \left(\frac{\mathcal{E}}{2}\right) \left(\frac{1-\eta}{1+\eta}\right)$$

$$\Rightarrow V_A - V_B = \left(\frac{\mathcal{E}}{2}\right) \left(\frac{1-\eta}{1+\eta}\right)$$

Q

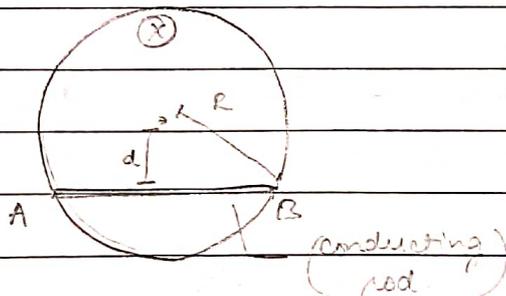

$$\frac{dB}{dt} = \alpha$$


find $V_A - V_B$

A. We assume a conducting loop

Since $E_i \perp OA$ & OB

\Rightarrow E_{induced} in OA & OB is ZERO

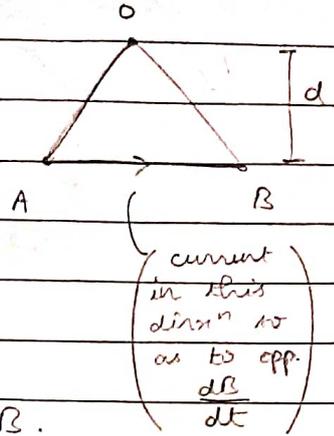\therefore all emf is induced across AB .



$$E = \frac{1}{2} (d) (2\sqrt{R^2 - d^2}) \alpha$$


$$\Rightarrow E_{AB} = -\alpha d \sqrt{R^2 - d^2}$$

(since pot. ↑ in dirn of induced)

Alternate Method

$$V_{AB} = \oint \vec{E}_i \cdot d\vec{l}$$

Q.

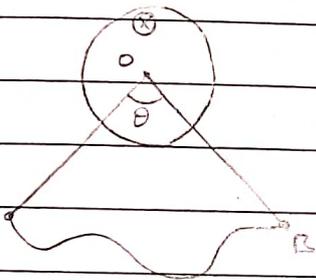

$$\frac{dB}{dt} = \alpha$$

Find $V_A - V_B$

A. By the argument we used in above Q,


E_{induced} in OA or OB is ZERO, \therefore all emf is induced across AB

$$E = \left(\frac{1}{2} \theta a^2 \right) \alpha$$

$$\Rightarrow E_{AB} = -\frac{\theta a^2 \alpha}{2}$$

2

Q.

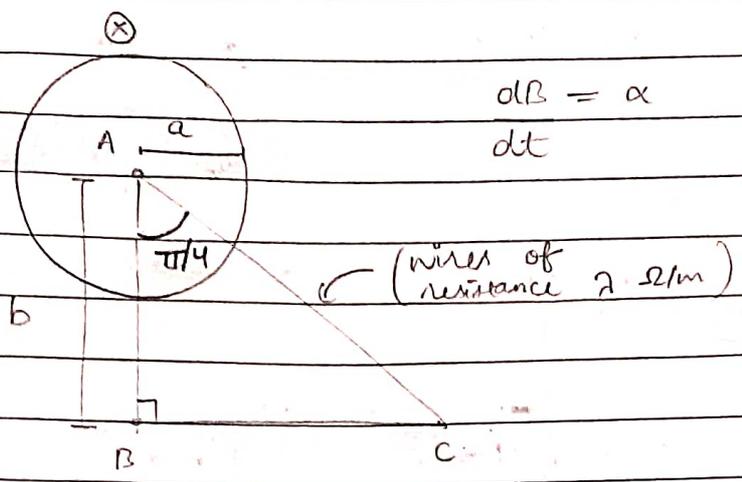


$$\frac{dB}{dt} = \alpha$$

Find $V_A - V_B$
 $V_B - V_C$

A.
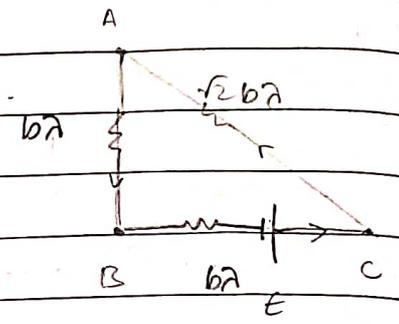
$$E = \frac{(\pi/4) a^2}{2} = \left(\frac{\pi a^2}{8}\right)$$




$$i = \frac{E}{(2+\sqrt{2})b\lambda} \Rightarrow V_B - b\lambda i + E = V_C$$


$$\Rightarrow V_B - V_C = b\lambda i - E$$

$$V_A - V_B = b\lambda i$$

Q.

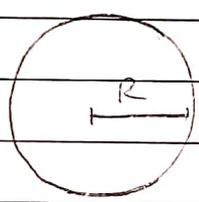

(m, q) uniform

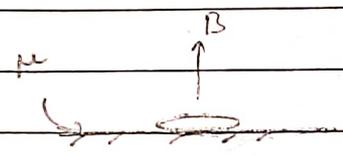

At $t=0$, a vertical B co-axial with conducting disc is switched on


$$B = B_0 t^2 T$$

- a) Find time t_0 when the disc will start rotating
- b) Find angular momentum of disc at $t = 2t_0$

$$(E_i) (2\pi r) = (\pi r^2) (2\dot{B}0t)$$

$$\Rightarrow E_i = B_0 r t$$

A. a)

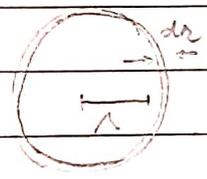

$$d\tau_{E_i} = dq E_i \quad \lambda = 2\pi \sigma_f \rho_0 r^3 t \quad dr$$

$$d\tau_{\mu} = \mu_0 dm \lambda = 2\pi \sigma_m \mu_0 q r^2 dr$$

Disc starts rotating when $\tau_{ei} = \tau_{fr}$

$$\Rightarrow \int_0^R 2\pi r \sigma_f \beta_0 t_0 r^2 dr = \int_0^R 2\pi r \mu_f r^2 dr$$

$$\Rightarrow \sigma_f \beta_0 t_0 \left(\frac{R^4}{4}\right) = \frac{\sigma_m \mu_f R^3}{3}$$

$$\Rightarrow t_0 = \left(\frac{\sigma_m}{\sigma_f}\right) \left(\frac{4\mu_f}{3\beta_0 R}\right) = \frac{4\mu_f \mu_g}{3\sigma_f \beta_0 R}$$


b) $\tau = \tau_{ei} - \tau_{fr} = \frac{q\beta_0 R^2}{2} t - \frac{2}{3} \mu_f m g R$

$$\Rightarrow \left(\frac{mR^2}{2}\right) \left(\frac{d\omega}{dt}\right) = \frac{q\beta_0 R^2}{2} t - \frac{2}{3} \mu_f m g R$$

$$\Rightarrow \int_0^{\omega} d\omega = \int_0^{t_0} \frac{q\beta_0}{m} t - \frac{4\mu_f}{3R} dt$$

(Rotⁿ starts after)
t = t₀
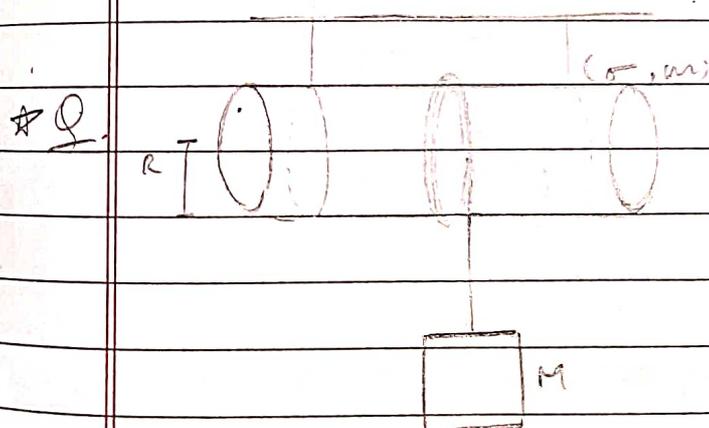
$$\Rightarrow \omega = \left(\frac{q\beta_0}{m}\right) \left(\frac{3t_0^2}{2}\right) - \frac{4\mu_f t_0}{3R}$$



Find ω as a fnⁿ of time.


A.

q rotates \rightarrow i created

B created \leftarrow (cylinder acts like solenoid)

$$\omega \uparrow \rightarrow i \uparrow \Rightarrow B \uparrow \Rightarrow \frac{d\Phi}{dt} \uparrow$$

(Provides torque) \leftarrow E_i created

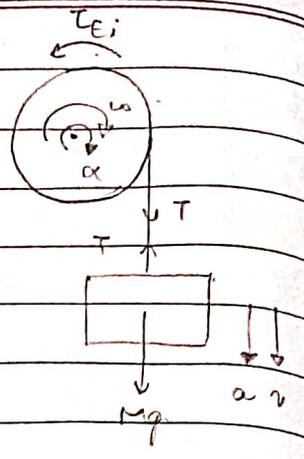

$$B = \mu_0 n i = (\mu_0) \left(\frac{N i}{L} \right) = \left(\frac{\mu_0}{L} \right) \left(\frac{q}{2\pi/\omega} \right) = \left(\frac{\mu_0}{L} \right) \left(\frac{\sigma \cdot 2\pi R L}{2\pi/\omega} \right)$$

$$= \mu_0 \sigma R \omega$$

$$E_i (2\pi R) = BA = (\mu_0 \sigma R \omega) (\pi R^2)$$

$$\Rightarrow E_i = \left(\frac{\mu_0 \sigma R^2}{2} \right) \omega$$

$$\tau = I \alpha \Rightarrow (m R^2) \alpha = \tau R = \int E \cdot R \cdot dq$$

$$\Rightarrow m R^2 \alpha = \tau R = E R \sigma 2\pi R L$$

Also, $Mg - T = Ma = MR\alpha \Rightarrow T = Mg - MR\alpha$

$$\Rightarrow m R^2 \alpha = MgR - MR^2 \alpha - \mu_0 \sigma R^3 L \omega^2 \alpha$$

$$\Rightarrow \alpha = \frac{MgR}{mR^2 + MR^2 + \mu_0 \sigma R^3 L \omega^2}$$

Since $\alpha = \text{const.} \Rightarrow v = at = R\alpha t$

$$\Rightarrow v = \left(\frac{Mg}{m + M + \mu_0 \sigma R L \omega^2} \right) t$$

10/08/2023

INDUCTANCE

- Resistor \rightarrow opposes current flow
 Capacitor \rightarrow opposes voltage change
 Inductor \rightarrow opposes magnetic flux change

Inductance is a geometrical ppt. i.e. does not depend on material of inductor.

When current is passed through a cond. loop, ϕ through it changes. $\Delta\phi$ induces an emf across the loop

This \mathcal{E}_i causes a current to flow in the loop. This phenomenon is known as self-inductance.

$$\mathcal{E}_i = -\frac{d\phi_c}{dt} = -L \frac{di}{dt}$$

(Coeff of self inductance)

SI unit: 1 Henry

or 1 Wb/A (weber/A)


or 1 T-m²/A

NOTE:

ϕ that we use while determining \mathcal{E}_i is not magnetic flux, rather it is linked magnetic flux.

We shall denote it by ϕ_c



eg - (i) Ring

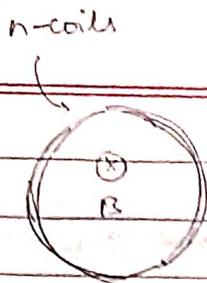

$$\phi = B \cdot A = \left(\frac{n \mu_0 i}{2R} \right) (\pi R^2)$$

Consider the emf induced in each coil
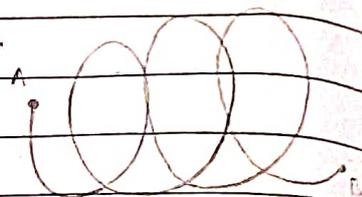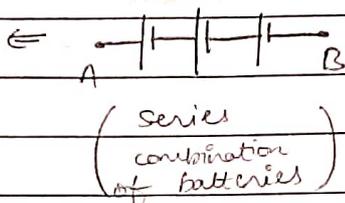
$$\begin{aligned} \epsilon_{i \text{ total}} &= n \epsilon_{i \text{ each coil}} \\ &= -n \left(\frac{d\phi}{dt} \right) \end{aligned}$$



Hence, we define ϕ_L s.t $\epsilon_{i \text{ total}} = -\frac{d\phi_L}{dt}$

$$\Rightarrow -\frac{d\phi_L}{dt} = -n \frac{d\phi}{dt} \Rightarrow \phi_L = n\phi$$


$$L \frac{di}{dt} = \frac{d\phi_L}{dt} \Rightarrow L_{\text{ring}} = \frac{d\phi_L}{di} = \frac{B(nA)}{i} = \frac{n^2 \mu_0 \pi R}{2} \quad \left(\begin{array}{l} \text{(\# loops)} \\ \text{(\# turns/length)} \end{array} \right)$$

(ii) Solenoid

$$\phi = n\phi$$

$$\Rightarrow L_{\text{solenoid}} = n \left(\frac{d\phi}{di} \right)$$

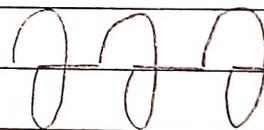
$$\Rightarrow L_{\text{solenoid}} = \pi r^2 \mu_0 n^2 l \quad \left(\begin{array}{l} \text{(\# turns/length)} \end{array} \right)$$



NOTE:

$$\epsilon_{\text{net}} = \epsilon/n = \frac{1}{n} \left(\frac{d\phi}{dt} \right) = \frac{d}{dt} \left(\frac{\phi}{n} \right)$$

$$\Rightarrow \phi_L = \frac{\phi}{n}$$

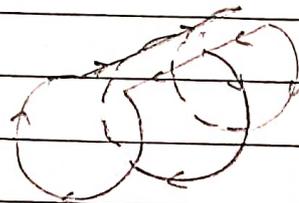

→ Mutual Inductance


If two loops are placed nearby & current is passed through one of them, $\Delta \phi$ induces \mathcal{E}_j in the other.

This phenomenon is known as mutual inductance

$$\frac{d\phi_2}{dt} = M_{12} \frac{di_1}{dt}$$

$$\frac{d\phi_1}{dt} = M_{21} \frac{di_2}{dt}$$

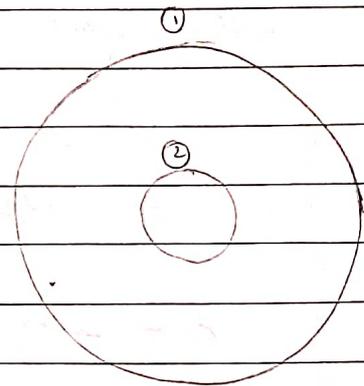(current change) \nearrow (linked flux change)



By Reciprocal then,

$$M_{21} = M_{12}$$


⇓

$$\phi_1 \text{ when } i \text{ through } 2 = \phi_2 \text{ when } i \text{ through } 1$$

To calc. M or ϕ , we choose which loop to pass current through as per our convenience.

Q 2 concentric coplanar rings have radii r & R ($r \ll R$). If i is passed through ring of radius r , find ϕ linked with ring of radius R .

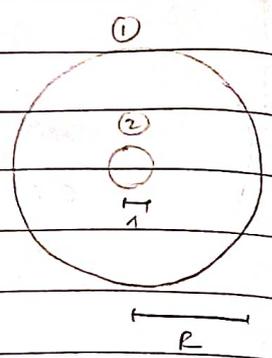A. ϕ_L through ① cannot be calc. directly as B is varying with space.



We instead pass i through ① to calc. E_i in ②


$$E_i = -M_{21} \frac{di}{dt} = -\frac{d\phi_L}{dt}$$

By Reciprocity Thm, $M_{21} = M_{12}$


$$\Rightarrow \frac{\phi_{12}}{i} = \frac{\phi_{21}}{i}$$

$$\Rightarrow \phi_{L1} = \left(\frac{\mu_0 i}{2R} \right) (\pi r^2) \quad \left[\text{assuming } B \text{ const as } r \ll R \right]$$

Q Find M_{12}

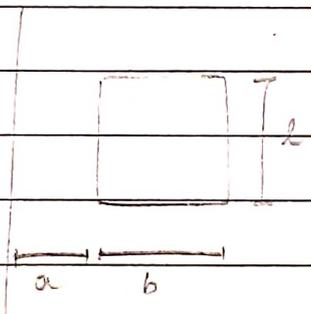

A.

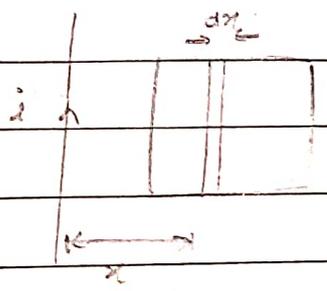


$$d\phi_L = \left(\frac{\mu_0 i}{2\pi x} \right) (l dx)$$

$$\Rightarrow \frac{\phi_L}{i} = \left(\frac{\mu_0 l}{2\pi} \right) \int_a^{(b+a)} \frac{dx}{x}$$

$$\Rightarrow M = \frac{\mu_0 l}{2\pi} \ln \left| \frac{b+a}{a} \right|$$

Q

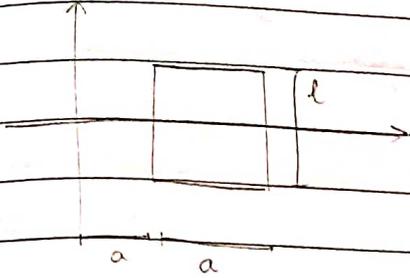


Find φ in x-y plane
for $x \leq -a$

A. We assume an ∞ wire at $x = -a$

By Reciprocity Thm,

$$\varphi_1 = \varphi_2 = \int_{-2a}^{-3a} dl dz$$

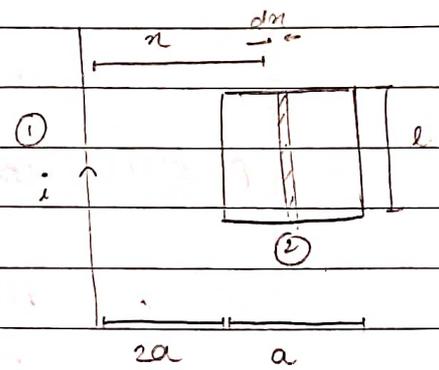
$$\Rightarrow \varphi_1 = \int_{-2a}^{-3a} \left(\frac{\mu_0 i}{2\pi r} \right) (l dx) = \frac{\mu_0 i l}{2\pi} \ln \left(\frac{3}{2} \right)$$



→ Inductor in circuit

$$\varphi = Li$$

$$\epsilon = -L \frac{di}{dt}$$

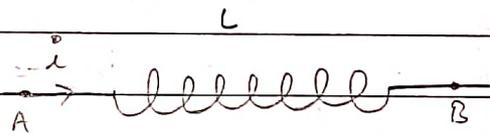


(Electronic symbol
for inductor)


$$\text{So, } V_A - L \frac{di}{dt} = V_B$$

• Series comb. -
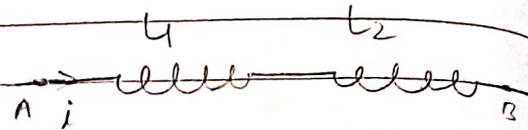
$$V_A - L_1 \frac{di}{dt} - L_2 \frac{di}{dt} = V_B$$



$$V_A - L \frac{di}{dt} = V_B$$

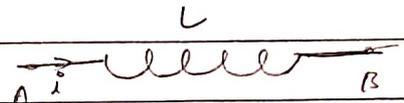


$$\Rightarrow \boxed{L = L_1 + L_2}$$


• Parallel Comb. -

$$\rightarrow i = i_1 + i_2$$
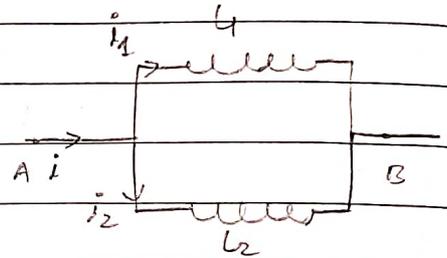
$$\rightarrow \frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$


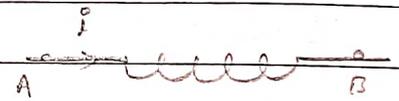
$$V_A - V_B = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} = L \frac{di}{dt}$$



$$\Rightarrow \boxed{\frac{1}{L} = \frac{1}{L_1} + \frac{1}{L_2}}$$



• Comb. of Inds with M.I -

Series)

$$\phi_1 = L_1 i + M i$$

(if ϕ in same dirⁿ)


$$\phi_2 = L_2 i + M i$$

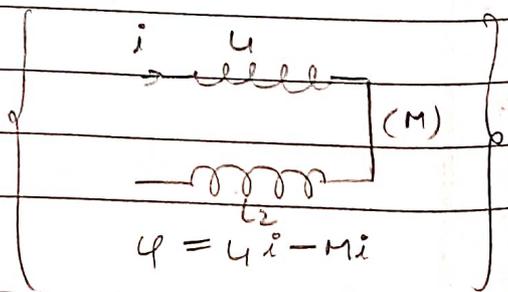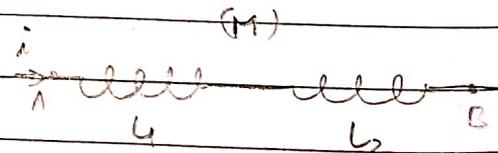

$$V_A - V_B = V_A - V_B \quad \equiv$$

$$\Rightarrow L \frac{di}{dt} = (L+M) \frac{di}{dt} +$$

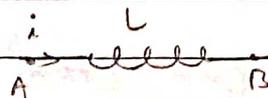
$$(L_2+M) \frac{di}{dt} \Rightarrow \boxed{L = L_1 + L_2 + 2M}$$



(Parallel)

$$i = i_1 + i_2$$

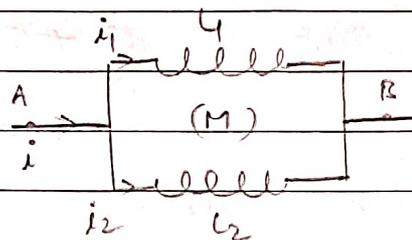
$$\Rightarrow \frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$



$$V_A - V_B = V_A - V_B$$

$$\Rightarrow L \frac{di}{dt} = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} - (i)$$
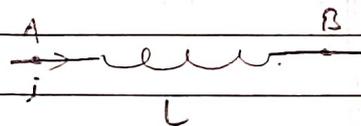
$$= L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} - (i)$$



$$L_2(i) - M(\dot{i}) \Rightarrow \frac{di_1}{dt} (L_1 L_2 - M^2) = L \frac{di}{dt} (L_2 - M)$$

Similarly

$$\frac{di_2}{dt} (L_1 L_2 - M^2) = L \frac{di}{dt} (L_1 - M)$$


$$\frac{1}{L} = \frac{L(L_2 - M)}{L_1 L_2 - M^2} + \frac{L(L_1 - M)}{L_1 L_2 - M^2}$$

$$\boxed{\frac{1}{L} = \frac{L_1 + L_2 - 2M}{L_1 L_2 - M^2}}$$

L-R CIRCUIT


Just after closing the switch, current through inductor will not change.

But $\frac{di}{dt} \neq 0$

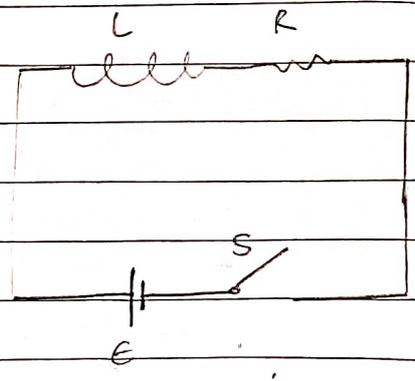

In steady state however, $\frac{di}{dt} = 0$


so inductor behaves as regular wire.

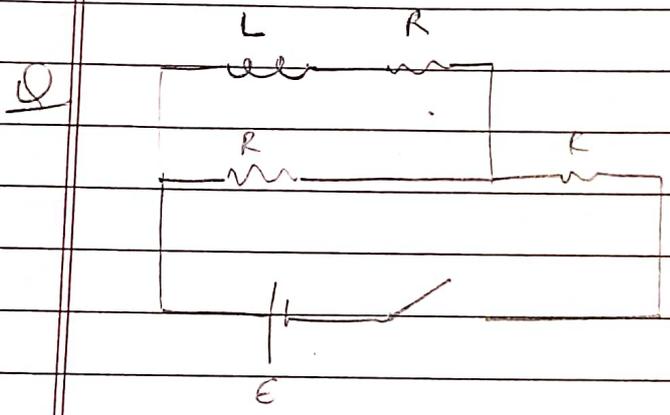

Switch closed at $t=0$
Find current through battery & V across ind.
a) just after closing switch
b) in steady state

A.

a)

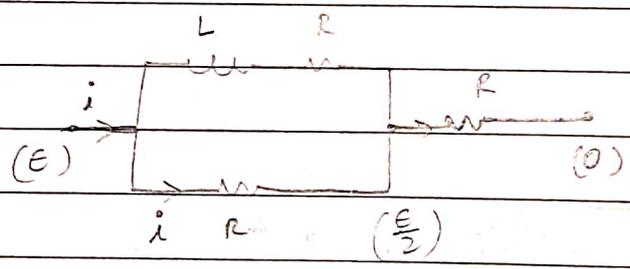


$$i = \frac{E}{2R}$$

0

$$V_R + V_L = \left(\frac{E}{2}\right) \Rightarrow \frac{di}{dt} = \frac{E}{2L}$$


b)

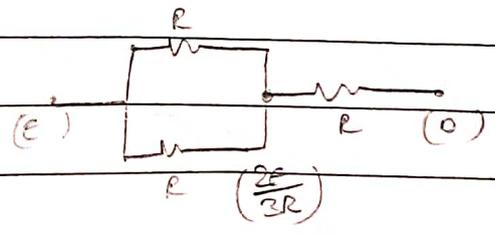

$$i = \frac{2E}{3R}$$


$$V_L = 0$$

Q.

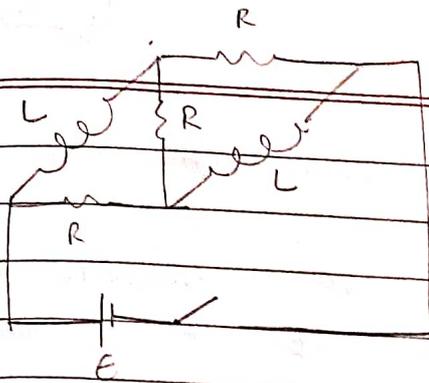


A.

a)

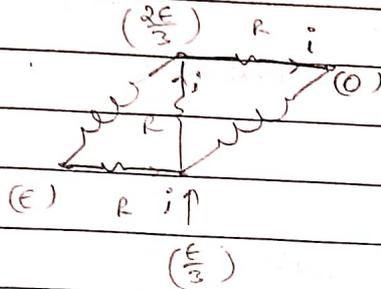


$$i = \frac{E}{3R} \Rightarrow V_L = \frac{E}{3}$$

b)

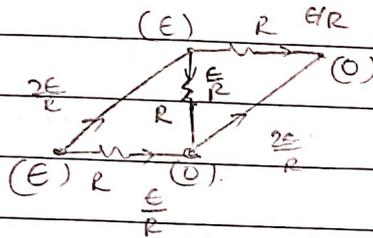

$$i = \left(\frac{3E}{R} \right)$$

Q.

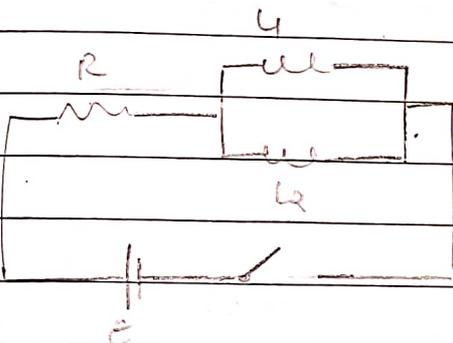

Find current through each inductor in steady state

A.

$$i = \frac{E}{R}$$

Since

$$V_{L1} = V_{L2}$$

$$\Rightarrow L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} \quad \forall t$$

$$\Rightarrow L_1 i_1 = L_2 i_2$$


$$\Rightarrow i_1 = \left(\frac{L_2}{L_1 + L_2} \right) \left(\frac{E}{R} \right)$$

$$i_2 = \left(\frac{L_1}{L_1 + L_2} \right) \left(\frac{E}{R} \right)$$



17/08/2023


Q.

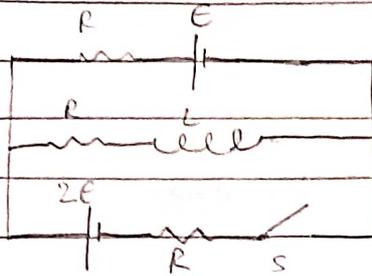

At $t=0$, the switch is closed.

Find the current through battery of $2E$ & V across the ind. just after closing the switch.

A.

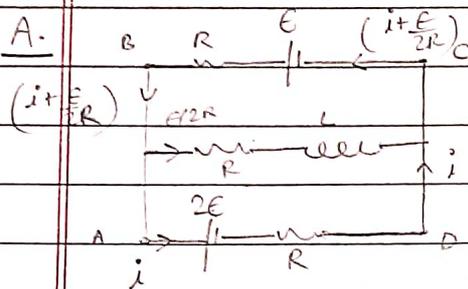

Initially $i = \frac{E}{2R}$ flowing through ind. (steady state)

When switch closed) no change in i through ind.

$$\text{In ABCD, } 2E + \left(i + \frac{E}{2R}\right)R - E + iR = 0$$

$$\Rightarrow \frac{3E}{2} = -2iR \Rightarrow i = -\frac{3E}{4R}$$


→ Growth & decay of current

$$-Ri - L \frac{di}{dt} + E = 0$$

$$\Rightarrow L \frac{di}{dt} = E - Ri$$



$$\Rightarrow \int_0^i \frac{di}{E - Ri} = \int_0^t \frac{dt}{L}$$
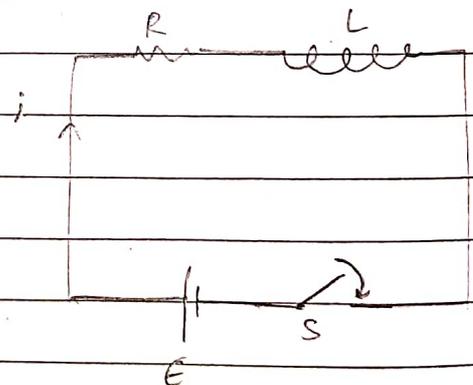
$$\Rightarrow \ln \left(\frac{E - Ri}{E} \right) = -\frac{Rt}{L}$$



$$\Rightarrow i = \frac{E}{R} \left(1 - e^{-\frac{t}{L/R}}\right)$$

Time const. (τ): $\tau = \frac{L}{R}$

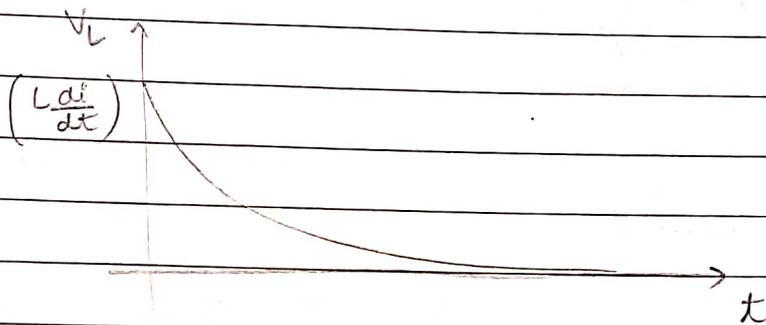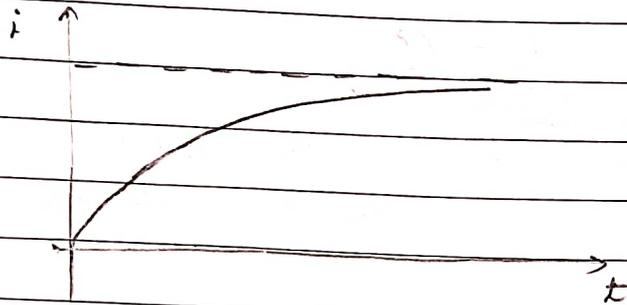



$$-L \frac{di}{dt} - Ri = 0$$

$$\Rightarrow \int_{i_0}^i \frac{di}{i} = - \int_0^t \frac{R}{L} dt$$

$$\Rightarrow \ln \left(\frac{i}{i_0} \right) = - \frac{Rt}{L}$$
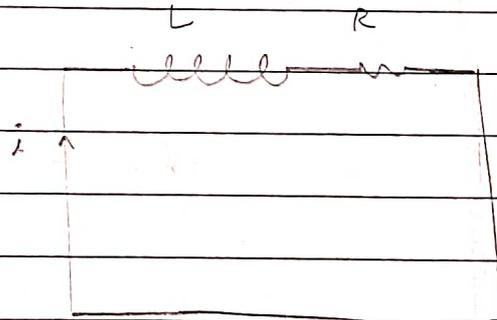
$$\Rightarrow i = i_0 e^{-\frac{t}{L/R}}$$



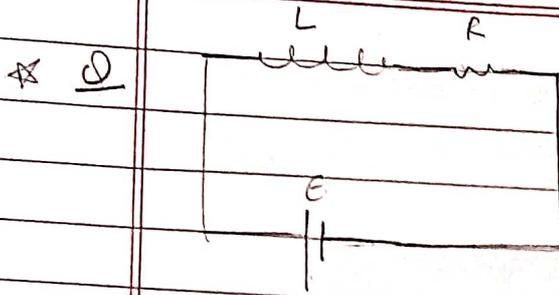


$$L \rightarrow \eta L \text{ at } t=0$$

Find current in circuit
as a fcnⁿ of time

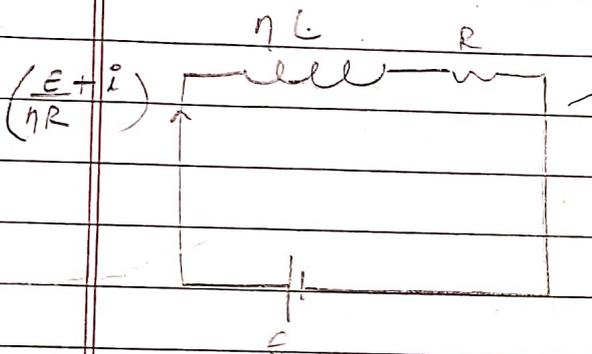A. Initially $i_L = \left(\frac{E}{R}\right)$

Since ind. tries to resist $\Delta\phi$,
changing L suddenly changes i s.t. $\Delta\phi = 0$

$$\Rightarrow i' = \left(\frac{E}{\eta R}\right)$$




$$-\eta L \frac{di}{dt} - R\left(\frac{E+i}{\eta R}\right) + E = 0$$

$$\Rightarrow \eta L \frac{di}{dt} + Ri = E\left(\frac{1+i}{\eta}\right)$$

$$\Rightarrow i = \frac{E(1+i)}{R\left(\frac{1}{\eta}\right)} \left(1 - e^{-\frac{Rt}{\eta L}}\right)$$


$$i(t) = i + \frac{E}{\eta R} = \left(\frac{E}{R}\right) \left(\frac{1}{\eta} + \left(\frac{1+i}{\eta}\right) \left(1 - e^{-\frac{Rt}{\eta L}}\right)\right)$$

Q.

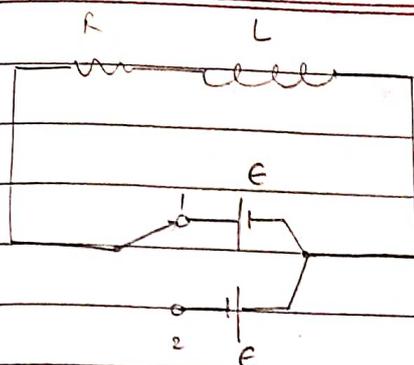

At $t=0$, switch moved from post. 1 to 2
find $i(t)$

A.

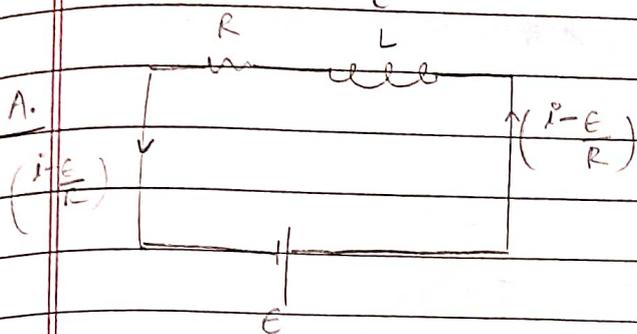


$$-L \frac{di}{dt} - R \left(i - \frac{E}{R} \right) + E = 0$$

$$\Rightarrow L \frac{di}{dt} + Ri = 2E$$

$$\Rightarrow i = \left(\frac{2E}{R} \right) \left(1 - e^{-\frac{t}{LR}} \right)$$


$$i(t) = i - \frac{E}{R} = \left(\frac{E}{R} \right) \left(1 - 2e^{-\frac{t}{L}} \right)$$

Q.

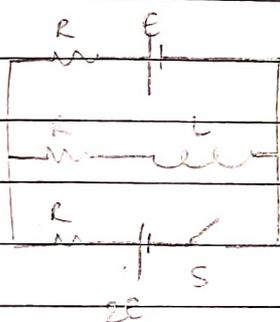

Switch closed at $t=0$.
find $i_L(t)$

A.

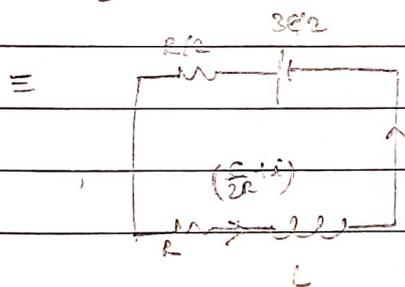


$$-\frac{3R}{2} \left(\frac{E+i}{2R} \right) - L \frac{di}{dt} + \frac{3E}{2} = 0$$

$$\Rightarrow L \frac{di}{dt} + \left(\frac{3R}{2} \right) i = + \frac{3E}{4}$$


$$\Rightarrow i = \left(\frac{+3E}{4} \right) \left(\frac{2}{3R} \right) \left(1 - e^{-\frac{3t}{2L}} \right)$$

$$= \frac{E}{2R} \left(1 - e^{-\frac{3t}{2L}} \right)$$
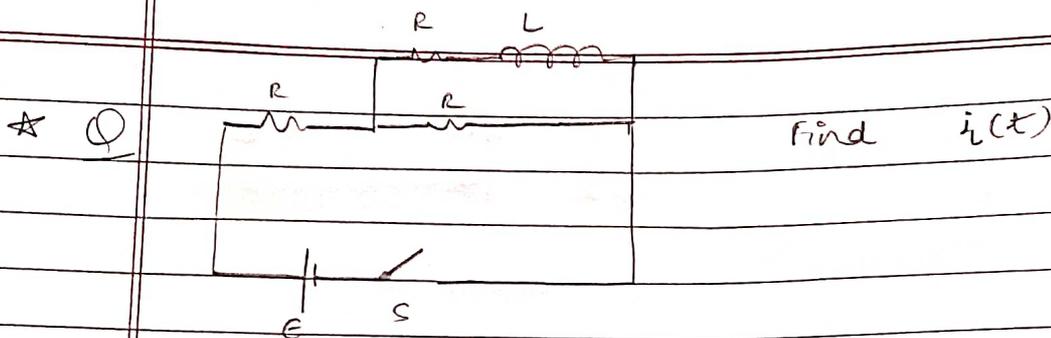
$$\Rightarrow i(t) = i + \frac{E}{2R} = \left(\frac{E}{2R} \right) \left(2 - e^{-\frac{3t}{2L}} \right)$$



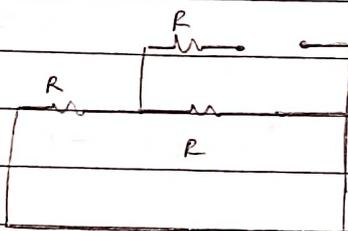A. To find τ , consider R_{eff} of circuit
abt L



$$\Rightarrow R_{eff} = 3R/2$$


$$\Rightarrow \tau = \frac{2L}{3R}$$

Steady state current through L is $\left(\frac{E}{3R}\right)$

$$\Rightarrow i_L(t) = \left(\frac{E}{3R}\right) \left(1 - e^{-\frac{3Rt}{2L}}\right)$$

→ Energy of Inductor

$$V_L = L \frac{di}{dt}$$

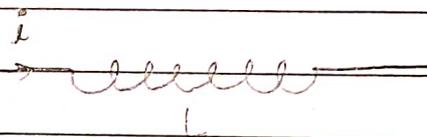


$$dW = V_L dq = L \frac{di}{dt} dq = L i di$$

$$\Rightarrow W = \int_0^i L i di = \frac{1}{2} L i_0^2 = \frac{\phi^2}{2L}$$

$$L = \mu_0 n^2 \pi R^2 l$$

$$U = \frac{1}{2} Li^2$$

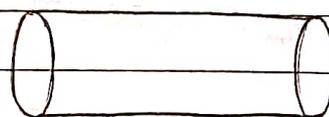

solenoid

$$u_B = \frac{U}{\text{Vol.}} = \frac{\mu_0 n^2 \pi R^2 l i^2}{2 (\pi R^2 l)}$$

(Energy density of B)


$$= \frac{B^2}{2\mu_0}$$

L-C OSCILLATION

i charges q till

$i \rightarrow 0$.

When $i=0$, $V_C = \frac{q}{C}$

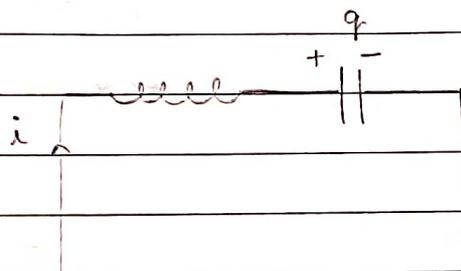

$\Rightarrow V_C = \frac{q}{C} \Rightarrow \frac{dq}{dt} = -\frac{q}{LC} \Rightarrow$ current starts flowing in opp. direction

So cap. starts discharging

Let us consider an L-C circuit with initial current i_0 & charge on cap. q_0 (changing current)

$$L \frac{di}{dt} + \frac{q}{C} = 0 \Rightarrow L \frac{d^2q}{dt^2} + \frac{q}{C} = 0$$

$$\Rightarrow \frac{d^2q}{dt^2} = -\left(\frac{1}{LC}\right) q$$

This is eqn of SHM \Rightarrow Charge performs SHM!

So

$$q = q_{\max} \sin(\omega t + \phi)$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\frac{dq}{dt} = q_{\max} \omega \cos(\omega t + \phi)$$

Given

$$q_0 = q_{\max} \sin(\phi)$$


$$i_0 = q_{\max} \omega \cos(\phi)$$

$$\Rightarrow \frac{q_0}{i_0} = \tan \phi \Rightarrow \phi = \tan^{-1} \left(\frac{q_0}{i_0} \right)$$

$$q_{\max} = \sqrt{q_0^2 + \left(\frac{i_0}{\omega} \right)^2}$$

Therefore,

$$q = \sqrt{q_0^2 + \left(\frac{i_0}{\omega} \right)^2} \sin \left(\frac{t}{\sqrt{LC}} + \tan^{-1} \left(\frac{q_0}{i_0} \right) \right)$$

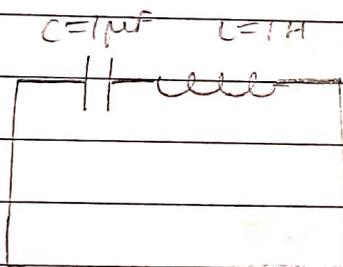Q.

at $t=0$, $q_0 = \sqrt{3} \mu\text{C}$
& $i_0 = 1\text{mA}$


find $q(t)$ & t_0 s.t. $i(t_0) = 0$ A.

$$\omega = 10^3 \Rightarrow q_{\max} = \sqrt{3+1} = 2 \mu\text{C}, \quad \phi = \tan^{-1} \left(\frac{\sqrt{3}}{1} \right) = \left(\frac{\pi}{3} \right)$$

$$q = 2 \sin \left(10^3 t + \frac{\pi}{3} \right) \mu\text{C}$$

When $i(t) = 0 \Rightarrow q = q_{\max} \Rightarrow 10^3 t + \left(\frac{\pi}{3} \right) = \left(\frac{\pi}{2} \right)$
 $\Rightarrow t = \frac{\pi \times 10^{-3}}{6}$

Q.

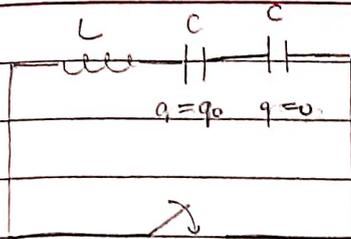

Find charge on uncharged cap. at a t^{th} of time.

A.

$$L \frac{di}{dt} - \frac{(q_0 - q)}{C} + \frac{q}{C} = 0$$

$$\Rightarrow \frac{2q}{C} - \frac{q_0}{C} = -L \frac{di}{dt} = -L \frac{d^2q}{dt^2}$$

$$\star \Rightarrow \frac{d^2}{dt^2} \left(\frac{q - q_0}{2} \right) = -\frac{2}{LC} \left(\frac{q - q_0}{2} \right)$$

$$\Rightarrow \frac{q - q_0}{2} = A \sin(\omega t + \phi) \quad ; \quad \omega = \sqrt{\frac{2}{LC}}$$


$$\Rightarrow i = A\omega \cos(\omega t + \phi)$$

$$i_0 = 0 \Rightarrow \phi = \left(\frac{\pi}{2} \right) \Rightarrow q = \frac{q_0}{2} + A \sin(\omega t + \pi/2)$$

$$q(0) = 0 \Rightarrow 0 = \frac{q_0}{2} + A \Rightarrow A = -\frac{q_0}{2}$$

$$\Rightarrow q = \frac{q_0}{2} (1 - \cos \omega t)$$

Q.

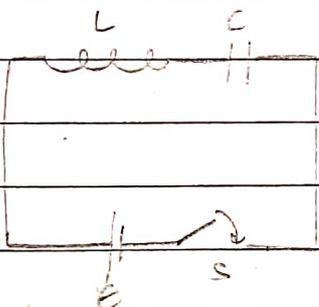


find $q(t)$ & $i(t)$

A.

$$E - L \frac{di}{dt} - \frac{q}{C} = 0$$
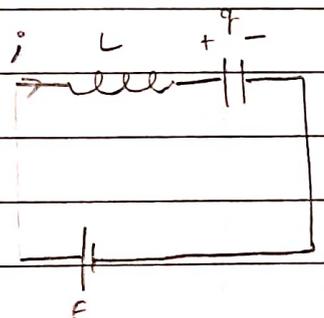
$$\Rightarrow \frac{1}{C} (q - EC) = -L \frac{d^2q}{dt^2}$$



$$\Rightarrow \frac{d^2 (q - EC)}{dt^2} = -\frac{1}{LC} (q - EC)$$

$$\Rightarrow q - EC = A \sin(\omega t + \phi) \quad , \quad \omega = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow i = A\omega \cos(\omega t + \phi)$$

$$i_0 = 0 \Rightarrow \phi = \pi/2$$

$$q_0 = 0 \Rightarrow 0 - EC = A \Rightarrow A = -EC$$

$$\Rightarrow q = EC (1 - \cos \omega t)$$

$$i = EC\omega \sin \omega t$$

→ Damped oscillation

(Damping const.)


$$m \frac{d^2 y}{dt^2} + b \frac{dy}{dt} + ky = 0$$

$$\Rightarrow y = A_0 e^{-\left(\frac{b}{2m}\right)t} \sin(\omega' t + \phi)$$

$$\omega' = \sqrt{\frac{k}{m} - \frac{b^2}{4m^2}}$$

$$A = A_0 e^{-\left(\frac{b}{2m}\right)t}$$

(Max. amp.)

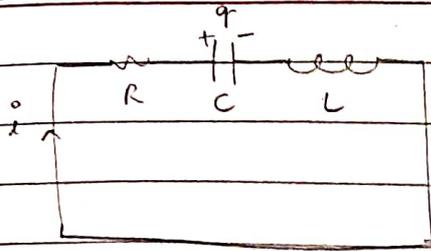


$$-iR - \frac{q}{C} - L \frac{di}{dt} = 0$$

$$\Rightarrow L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0$$

$$\Rightarrow q = q_0 e^{\left(\frac{-Rt}{2L}\right)} \sin(\omega t + \phi)$$

$$q_{\max} = q_0 e^{\left(\frac{-Rt}{2L}\right)}$$

(max. max. charge)

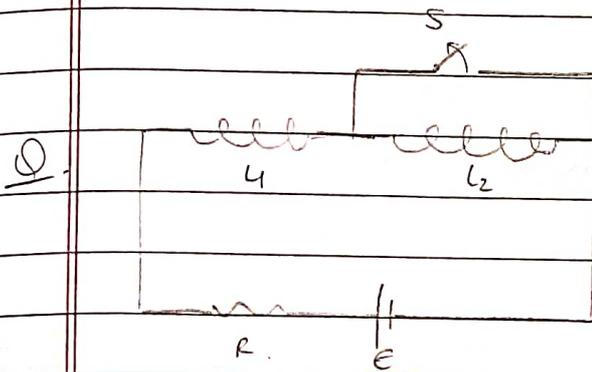

Find current immediately after opening S. & in new steady state

A.

$$i = \left(\frac{E}{R}\right)$$


Ind. changes current to conserve flux of circuit.

$$\Rightarrow (L_1 + L_2)(i) = L_1 i'$$

$$\Rightarrow i' = \left(\frac{L_1}{L_1 + L_2}\right) \left(\frac{E}{R}\right)$$

$$i_s = \left(\frac{E}{R}\right)$$

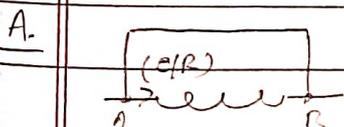* Q. In the above Q, if S closed again, find i, just after closing the switch



$V_{AB} = 0$
 $V_{AB}' = 0$
(after closing switch)

\Rightarrow NO current through wire

\Rightarrow No flux change in inductor!

\Rightarrow same i as in steady state